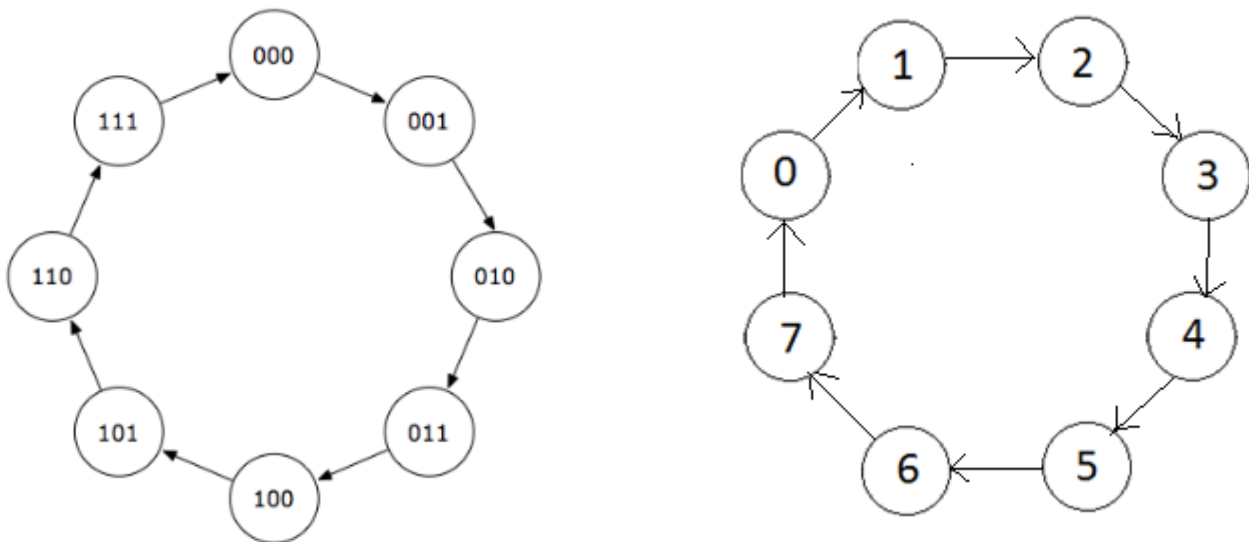


## FSM (8 STATES).

## SYNCHRONE 8-TELLER MET D-FF



Given is the FSM with 8 states. This is a synchronous counter. The system has no inputs (except for the clock and probably an asynchronous reset). At each active edge it goes to the next state. The system is realized with 3 D flip-flops,  $Q_2$ ,  $Q_1$  and  $Q_0$ . (The flip-flop outputs are also the outputs of the system).

Determine the Boolean equations for the combinational logic for the data inputs of these flip-flops.

Ontwerp een synchrone 8-teller met D-FF

Excitatie tabel D-FF		
$Q_n$	$Q_{n+1}$	$D_n$
0	0	0
0	1	1
1	0	0
1	1	1

Volgordetabel synchrone 8-teller met 3 D-FF (Excitatie tabel)											
Voor de klokpuls $Q_n$			Na de klokpuls $Q_{n+1}$				D-ingang				
decimaal	$C_n$	$B_n$	$A_n$	$C_{n+1}$	$B_{n+1}$	$A_{n+1}$	decimaal	$D_{Cn}$	$D_{Bn}$	$D_{An}$	
0	0	0	0	0	0	1	1	0	0	1	
1	0	0	1	0	1	0	2	0	1	0	
2	0	1	0	0	1	1	3	0	1	1	
3	0	1	1	1	0	0	4	1	0	0	
4	1	0	0	1	0	1	5	1	0	1	
5	1	0	1	1	1	0	6	1	1	0	
6	1	1	0	1	1	1	7	1	1	1	
7	1	1	1	0	0	0	0	0	0	0	

		BA		$D_{Cn}$	
C		00	01	11	10
0		0	0	1	0
1		1	1	0	1


		BA		$D_{Bn}$	
C		00	01	11	10
0		0	1	0	1
1		0	1	0	1

		BA		$D_{An}$	
C		00	01	11	10
0		1	0	0	1
1		1	0	0	1

$$D_{Cn} = C\bar{B} + C\bar{A} + ABC\bar{C}$$

$$D_{Bn} = A\bar{B} + \bar{A}B = A \oplus B = (XOR)$$

$$D_{An} = \bar{A}$$

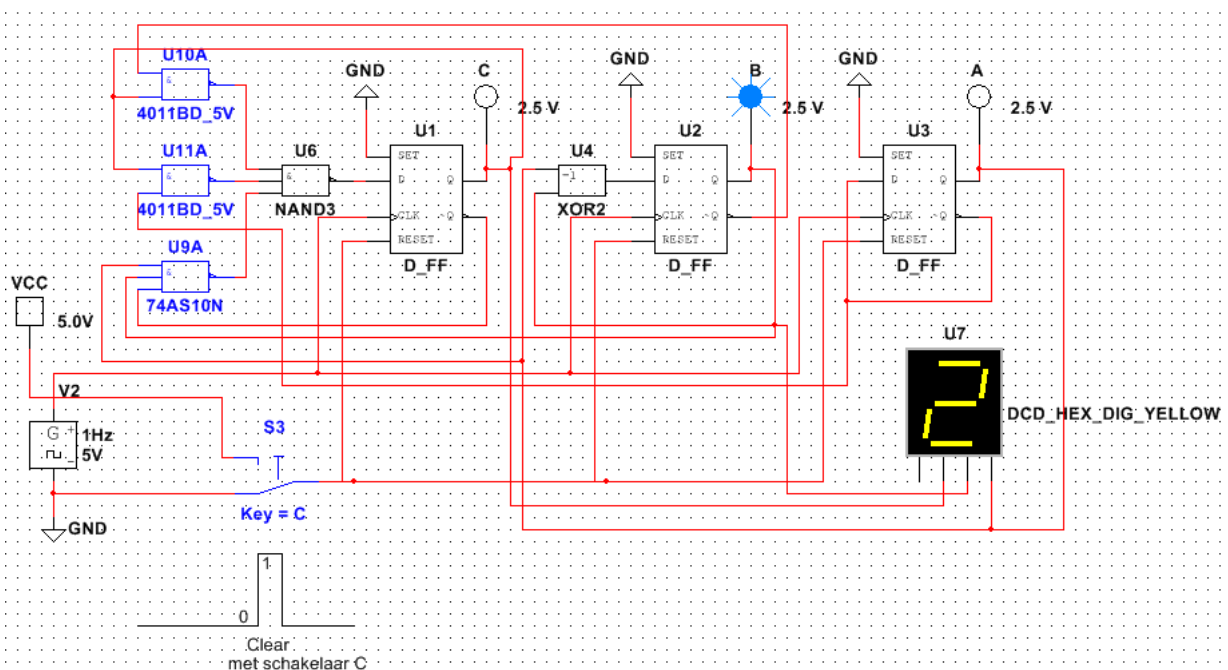

Ontwerp een synchrone 8-teller met D-FF

	00	01	11	10
0				
1				

	00	01	11	10
0				
1				

	00	01	11	10
0				
1				

	00	01	11	10
0				
1				

	00	01	11	10
0				
1				

	00	01	11	10
0				
1				

	00	01	11	10
00				
01				
11				
10				

	00	01	11	10
00				
01				
11				
10				

	00	01	11	10
00				
01				
11				
10				

	00	01	11	10
00				
01				
11				
10				

	00	01	11	10
00				
01				
11				
10				

	00	01	11	10
00				
01				
11				
10				

	00	01	11	10
00				
01				
11				
10				

	00	01	11	10
00				
01				
11				
10				

	00	01	11	10
00				
01				
11				
10				